

Alternate diode voltage search method using Newton-Raphson

Cory Lanker

2023-06-14

Introduction

Calculating the diode voltage is difficult in even a simple circuit consisting of a voltage source of 1.45 V, a resistor of 4246.4 Ω , and diode with $I_S = 2$ fA. The diode current is $I_D = I_S e^{V_D/V_T}$ and is equal to the current through the resistor $(V_x - V_D)/R$.

Methods

Solution 1 with exponential term for V_D

Newton-Raphson can solve for the unknown V_D when setting these terms equal. The difference between these terms is zero and provides the function to solve

$$f(V_D) = I_S e^{V_D/V_T} - \frac{1}{R}(V_x - V_D),$$

with derivative

$$f'(V_D) = \frac{I_S}{V_T} e^{V_D/V_T} + \frac{1}{R}.$$

Solution 2 after taking logarithm

An interesting alternative solution that converges much quicker is taking the log of the terms to derive the solving function $g(V_D)$ as follows:

$$I_S e^{V_D/V_T} = \frac{1}{R}(V_x - V_D)$$

$$\log(I_S) + \frac{1}{V_T} V_D = \log(V_x - V_D) - \log(R),$$

leading to

$$g(V_D) = \log(V_x - V_D) - \frac{1}{V_T} V_D - \log(I_S R)$$


and corresponding derivative

$$g'(V_D) = -\frac{1}{V_x - V_D} - \frac{1}{V_T}.$$

Results


Comparing the first iteration V_D values based on the initial guess $V_{D,0}$, noting that V_D is 0.65676.

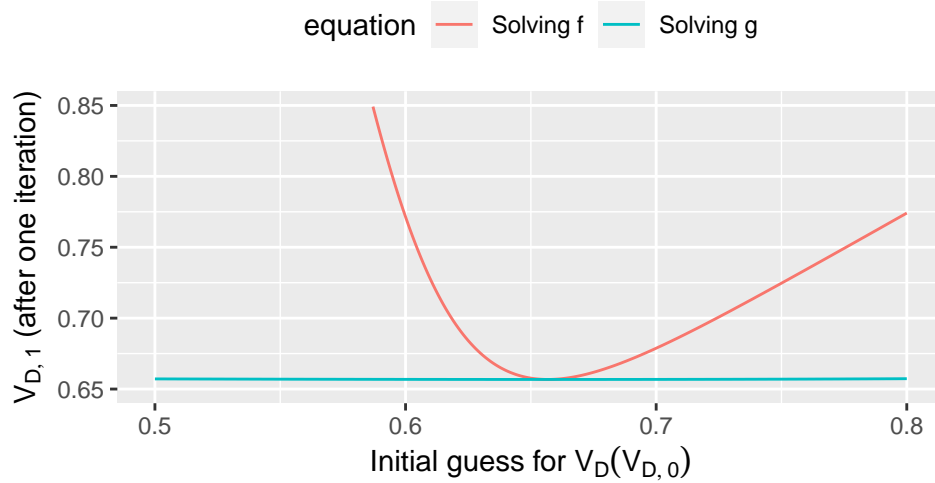Showing the single iteration Newton–Raphson results



A zoom-in on the solution with $g(V_D)$ shows how accurate a single iteration is for the logarithm method.

Zoom in around correct $V_D = 0.65676$

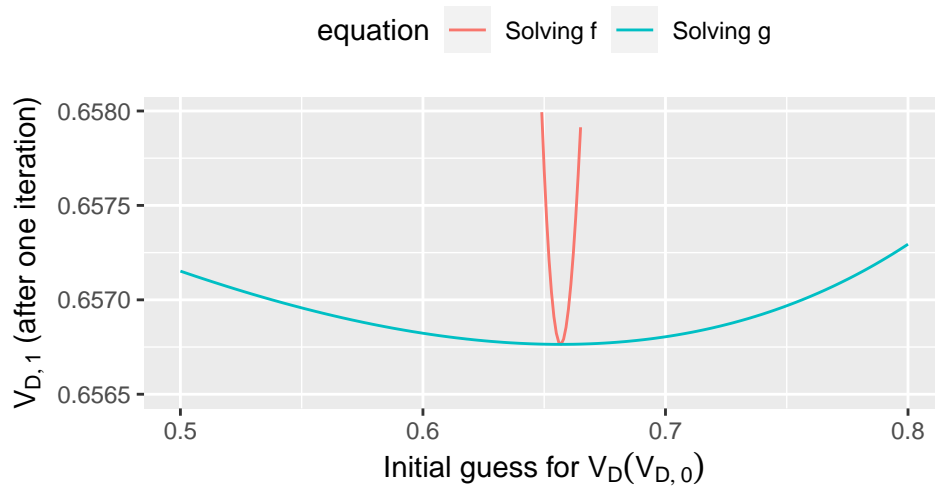


Discussion

The Newton-Raphson algorithm converges much quicker if the derivative equation $f'(V_D)$ changes less over the range of V_D . E.g., an equation $f(V_D)$ with constant derivative (i.e., linear function) would get an exact solution after one iteration. Therefore the less the derivative $f'(V_D)$ changes versus V_D , the quicker the convergence.

Here is a plot of the derivatives $f'(V_D)$ and $g'(V_D)$ over the range of V_D .

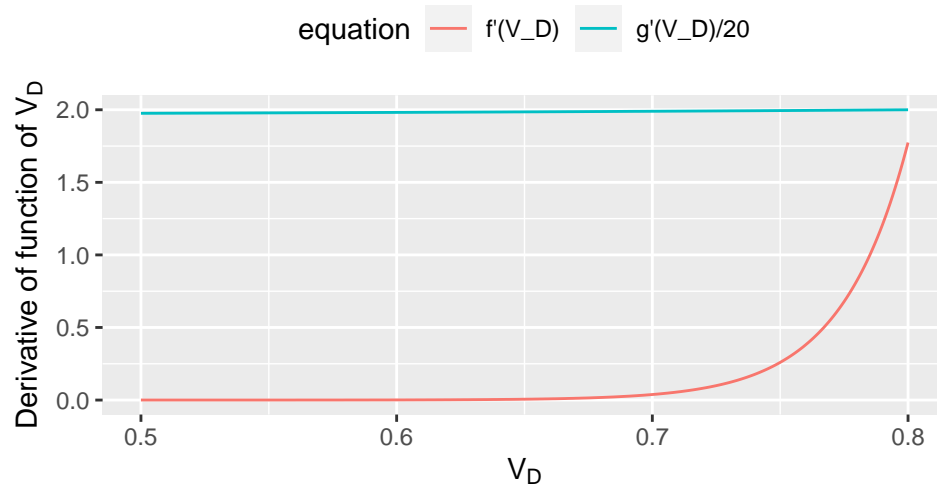Showing the derivative of the solving functions



As the derivative changes less drastically with $g(V_D)$, its solutions converge much quicker.